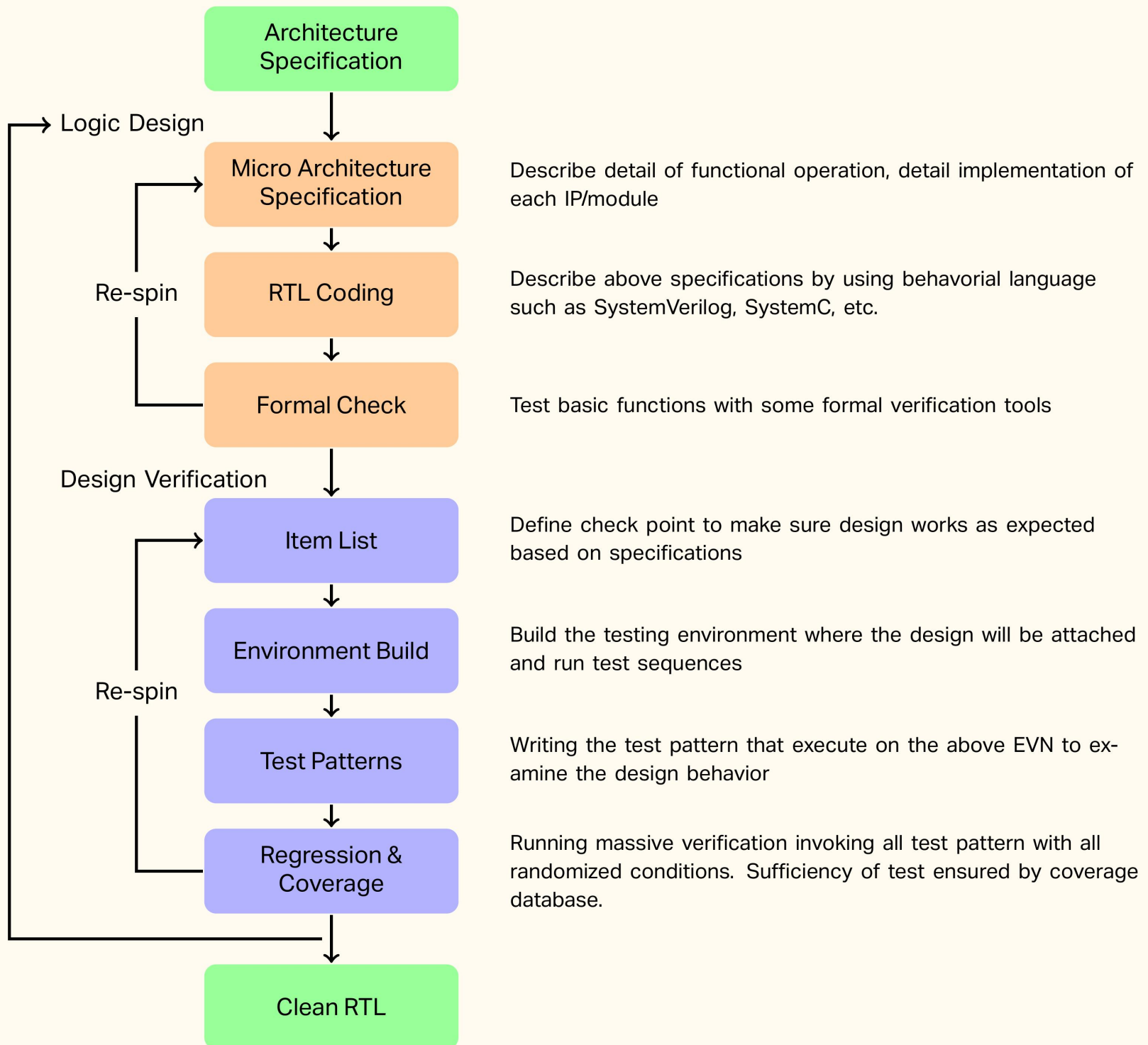


System Verilog 101

Presenter: Hai Cao Xuan

Computer Architecture 203B3





objectives

- Understand basics of SystemVerilog
- Understand how to model combinational logic
- Understand how to use `always_comb` and `always_ff`
- Understand the difference between blocking and non-blocking assignments
- Understand how to analyze FSMs
- Understand how to model basic components: Counter, Register, RAM
- Apply the coding guideline when coding

Gate-level Combinational Modeling

modules



Module is the basic building block in SystemVerilog.

Every module usually defines:

- Input ports → Input signals of the circuit
- Output ports → Output signals of the circuit
- Concurrent statements → Logic of the circuit

modules

Exercise 1a. 2-1 Multiplexer

  

Netlist

Yosys

To view the schematic of your design, create a *.ys file, then run:

```
$ yosys file.ys
```

```
$ netlistsvg -o file.svg file.json
```

An *.svg will be in the folder, you could open it using your browser.

```
$ brave file.svg
```


modules

Logic data type

Use logic instead of wire and reg: **0**, **1**, **x**, **z**

Vectors

Signals can be declared as vectors using **[N:0]** notation.

For example:

- an 8-bit vector → **logic [7:0]**
- an N-bit vector → **logic [N-1:0]**

Access the *i*th bit with **[i]**, or a bit slice from *j*th to *i*th with **[i:j]**

modules



Module instantiations

Reusing other modules in a “big” module is frequent.

→ See the example to know how to use this.

modules

Exercise 1b. 4-1 Multiplexer

  

Guideline

→ *Naming*

Declarations

lower_snake_case

Instance names

lower_snake_case

Signals (nets or ports)

lower_snake_case

→ *Suffixes for signal names*

Input

signal_i

Output

signal_o

Inout

signal_io

Active low

signal_n

Active high (if active low is present)

signal_p

? Input active low

signal_ni

literals

Binary → b: 0, 1

Decimal → d: 0, 1, 2, 3, 4, 5, 6, 7, 8, 9

Hexadecimal → h: 0, 1, 2, 3, 4, 5, 6, 7, 8, 9, A, B, C, D, E, F

A literal may contain x or z.

A literal could be signed or unsigned, using "s"

literals

16'd8 → Decimal → Unsigned → 16 bits

16'sd9 → Decimal → Signed → 16 bits

4'b1011 → Binary → Unsigned → 4 bits

10'h2FA → Hexadecimal → Unsigned → 10 bits

12'b0110_0010_1101 → Use underscores for more readable

'0 → depend on the width of signal → N'b00...00

'1 → depend on the width of signal → N'b11...11

RT-level Combinational Modeling

continuous assignments

assign binds an expression (right-hand) to a signal (left-hand).

assign [signal] = [expression]

and (c_o, a_i, b_i) \rightarrow assign c_o = a_i & b_i

Continuous assignments are continuous, so these two are equal:

logic [2:0] a;	logic [2:0] a;
logic b;	logic b;
logic tmp;	logic tmp;
assign tmp = a[0] a[1];	assign b = tmp ^ a[2];
assign b = tmp ^ a[2];	assign tmp = a[0] a[1];

continuous assignments

Bitwise operators

`assign c[0] = a[0] | b[0];` → `assign c = a | b;`

`assign c[1] = a[1] | b[1];`

and → `&`, or → `|`, xor → `^`, not → `~`

Reduction operators

`assign b = a[0] & a[1] & a[2];` → `assign b = &a;`

and → `&`, or → `|`, xor → `^`, nand → `~&`, nor → `~|`, xnor → `~^`

Logical operators

Only produce true or false (1 bit) → Should use for scalar values/signals (true/false)

and → `&&`, or → `||`, not → `!`

continuous assignments

Shift operators

left logical \rightarrow `<<`, right logical \rightarrow `>>`, right arithmetic \rightarrow `>>>`

Arithmetic operators

add \rightarrow `+`, subtract \rightarrow `-`,

multiply \rightarrow `*`, divide \rightarrow `/`, modulus \rightarrow `%`, power \rightarrow `**`

Conditional operator

`mux mux (a_i, b_i, sel_i, c_o) \rightarrow assign c_o = sel_i ? b_i : a_i;`

`condition ? result_if_true : result_if_false`

continuous assignments

Comparison operators

equal \rightarrow `==`, less than \rightarrow `<`, less than or equal \rightarrow `<=`
not equal \rightarrow `!=`, greater than \rightarrow `>`, greater than or equal \rightarrow `>=`

Concatenate and replicate operators

`{a,b}` concatenate vector a with vector b
`{n{a,b}}` concatenate vector a with vector b and replicate the result n times
 \rightarrow `{n{a},b}` replicate vector a n times and concatenate with vector b

parameter and localparam

parameter the constant could be modified when instantiating

localparam the constant is "local" to the module

```
module module_name #(
    parameter UpperCamelCase      = ...,
    parameter AnotherUpperCamelCase = ...
) (
    ...
);
```

```
    localparam ALL_CAPS          = ...;
    localparam ANOTHER_ALL_CAPS = ...;
```

```
...
```

```
endmodule : module_name
```

Guideline

→ *Naming*

Tunable Constants (parameter)


UpperCamelCase

True Constants (localparam)

ALL_CAPS

modules

 Exercise 1c. 2-1 Multiplexer N-bit (configurable)



generate

generate helps create replicated structure.

generate

genvar [index_variables];

for ([initial]; [condition]; [inc/dec]) **begin** [: optional_label]

 [...concurrent_statements...]

end

endgenerate

assign c[0] = a[0] | b[0]; →

assign c[1] = a[1] | b[1];

...

assign c[N] = a[N] | b[n];

generate

genvar i;

for (i = 0; i < N; i++) **begin** : gen_or

assign c[i] = a[i] | b[i];

end

endgenerate

always_comb

always_comb helps create combinational logics conveniently.

It is highly recommended than **always @(*)**

```
always_comb begin [: optional_label]  
    [optional_local_variable_declarations]  
    [...procedural_statements...]  
end
```

This coding style is preferred.

```
logic [N-1:0] a;  
always_comb begin : proc_example  
    a = '0; // default value  
    if (sel)  
        a = b + c;  
end
```


always_comb – blocking assignments

The value of the expression is evaluated and assigned to the variable/signal immediately

→ Next procedural statements will use that variable → Blocking

```
[variable_name] = [expression]; // blocking assignment
```

Should be used for always_comb only, aka combinational logic.

Compare these two

```
initial x = 0;  
always_comb begin  
    x <= 2;  
    y <= x + 1;  
end
```

```
initial x = 0;  
always_comb begin  
    y <= x + 1;  
    x <= 2;  
end
```

always_comb – if statements

```
if ([boolean]) begin  
    [...procedural_statements...]  
end else begin  
    [...procedural_statements...]  
end
```

```
if ([boolean]) begin  
    [...procedural_statements...]  
end
```

Remember **always assign default** values to signals/variables, especially when just one “if” is used.

always_comb – case statements

```
case [expression]
  [item]: begin
    [procedural_statements]
  end
  [item]: begin
    [procedural_statements]
  end
  ...
  default: begin
    [procedural_statements]
  end
endcase
```

Remember **always assign default** values to signals/variables, All cases should be considered.

Modeling Sequential Circuits

always

always uses a sensitivity list to perform value changes.

```
always @([sensitivity_lists]) begin [: optional_label]  
    [optional_local_variable_declarations]  
    [...procedural_statements...]  
end
```

For example, sum will change if a or b change their values.

```
always @(a, b) begin : proc_example  
    sum = a + b;  
end
```

The sensitivity list uses the **posedge** or **negedge** keyword in front of a signal to specify the edge transition of that signal.

The wildcard * means all signals in all expressions of procedural statements are in the sensitivity list. → Look like another way to model combinational logic → **but should not use**

always – non-blocking assignments

The value of the expression is evaluated and assigned to the variable/signal at the end of always block.

- Previous procedural statements will not block the following ones.
- Not assign a value at least twice
- Use non-blocking assignments to model sequential logic

```
[variable_name] <= [expression]; // non-blocking assignment
```

```
initial x = 0;  
always @(posedge clk) begin  
    x = 2;  
    y = x + 1;  
end  
→ x = 2, y = 3
```

```
initial x = 0;  
always @(posedge clk) begin  
    y = x + 1;  
    x = 2;  
end  
→ x = 2, y = 1
```

always_ff

always_ff notices the compiler the intention of synthesizing flip-flops uses a sensitivity list to perform value changes.

→ Use this instead of plain always



```
always_ff @([sensitivity_lists]) begin [: optional_label]  
    [optional_local_variable_declarations]  
    [...procedural_statements...]  
end
```

```
always_ff @(posedge clk) begin : proc_example  
    if (sel)  
        a <= b + c;  
end
```

modules

Exercise 2a. DFF with enable signal

Exercise 2b. 2-DFF Synchronizer

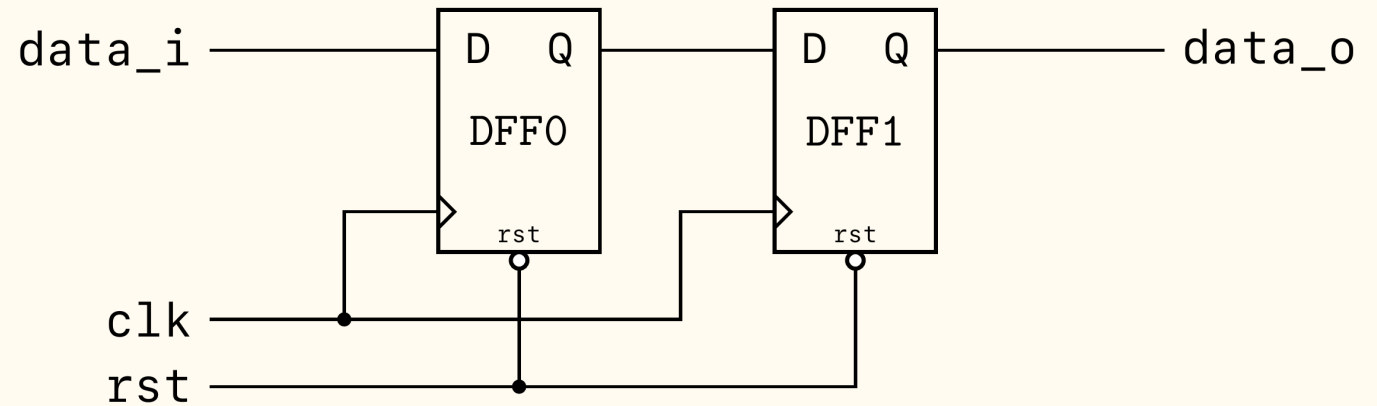 

Guideline

→ *Prefixes for optional label*

generate

gen_

always...

proc_

sequential circuit

A general block diagram of a sequential logic contains:


- State register → Flipflop
- Next-state logic → Combinational circuit
- Output logic → Combinational circuit

Modeling Finite State Machines

diagram and implementation

Moore machine → The output depends on the state only.

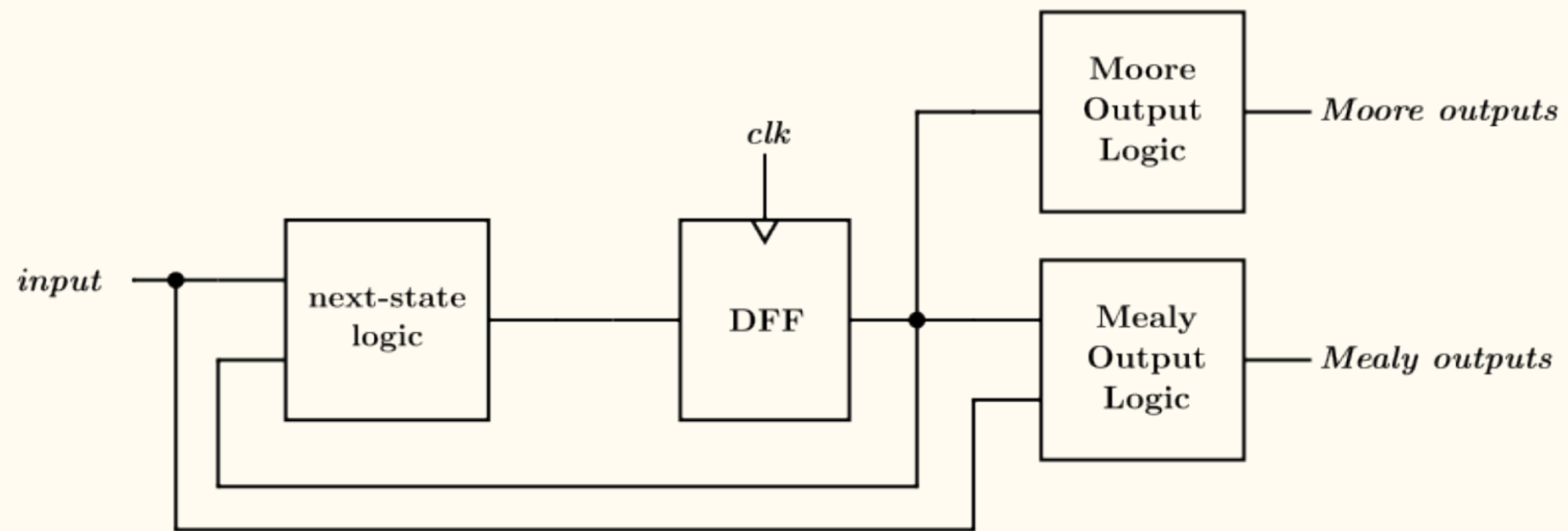Mealy machine → The output depends on the state and the input.



enum – enumerations

If **logic** only has 4 states: 0, 1, x, z, **enum** helps create more.

typedef is to create user-defined data type.

```
typedef enum [storage_type]{  
    [state_name] [= state_value,]  
    [state_name] [= state_value,]  
    ...  
    [state_name] [= state_value]  
} [new_name_type];
```

An FSM has three states: IDLE, PAUSE, ADD

```
typedef enum logic [1:0] {  
    S_IDLE = 2'b00;  
    S_PAUSE = 2'b01;  
    S_ADD = 2'b10;  
} state_e;  
state_e current_state, next_state;
```

Guideline

→ *Suffix*

enum

_e


modules

Exercise 3. Universal counter

Two modes: Add and Subtract (by 1)

Counter only works when $en = 1$, or it will hold the current data.

Counter has an active low reset.

 

Modeling Memory

array

Packed Array

- Of single bit data types (logic), enumerated types, and even packed arrays

```
logic [7:0][3:0] array0;
```

```
state_e [2:0] state_array;
```

```
logic [3:0][7:0][3:0] packed_array;
```

- One dimensional packed array → vector → convenient to access a bit or bit slice

```
array0[2]; array0[3][5:3]; array0[1][1];
```

- Represented as a contiguous set of bits

array

Unpacked Array

- Of any data types

```
logic uarray0[7:0][3:0];
```


```
state_e state_uarray[5:0];
```

```
logic [3:0][7:0] mix[3:0];
```

- Not guaranteed to be represented as a contiguous set of bits

array

logic [1:0][7:0] regs [0:3][0:2]

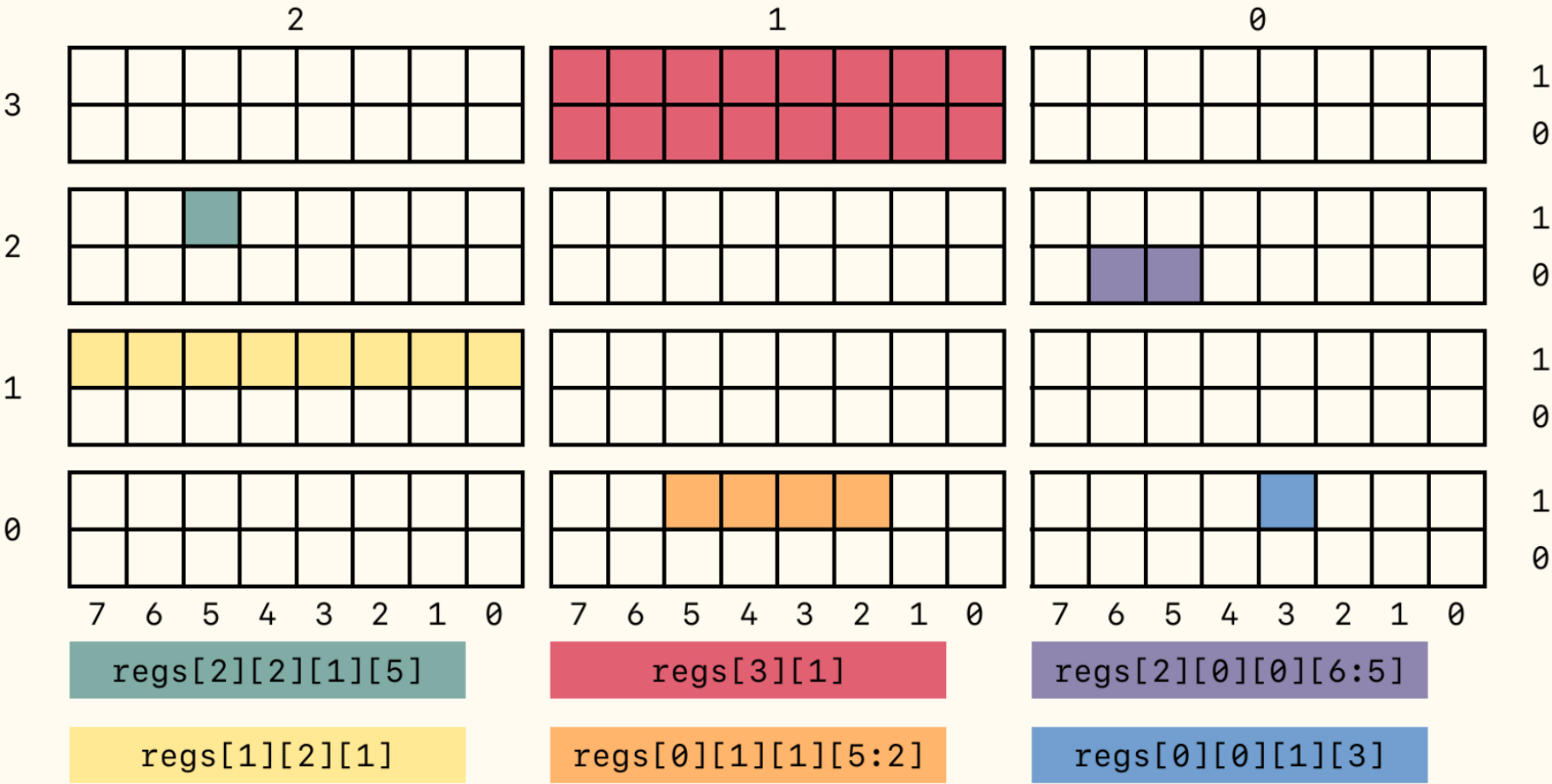

RAM and register file

Exercise 4a. Single-port RAM

Exercise 4b. Dual-port RAM

Exercise 4c. Regfile

A Little Bit Advanced

signal clusters

```
typedef struct packed{  
    [storage_type] [signal];  
    [storage_type] [signal];  
    ...  
    [storage_type] [signal];  
} [cluster_type];
```

A module requires logic operator data and 2 operands. It could be configured as 1 data:

```
typedef struct packed{  
    logic [2:0] logic_operator;  
    logic [7:0] operand_a;  
    logic [7:0] operand_b;  
} logic_data_s;
```

```
logic_data_s data_in;
```

```
assign lu_op = data_in.logic_operator; // use "." to access data
```

Guideline

→ *Suffix*

signal clusters

_s

other typedef

_t

package and *.svh files

When working on large projects, a number of parameters or types (enum, struct,...) will become global.

→ Painful if declaring them again and again in each module file

→ Modify one → Modify all

```
package [package_name];  
    [declarations];  
endpackage [: package_name]
```

→ Create *.svh files to store only packages

→ **parameter** will be declared in package → global

→ **localparam** will be in the specific module → local

Questions?

References

1. <https://github.com/lowRISC/style-guides/blob/master/VerilogCodingStyle.md>
2. https://zyedidia.github.io/notes/sv_guide.pdf
3. http://courses.eees.dei.unibo.it/LABMPHSENG/wp-content/uploads/2016/02/SystemVerilog_3.1a.pdf